

**16-bit ALU simulation, Phase1: 1-bit ALU simulation**

As the first step of simulating a 16-bit ALU, which performs AND, OR, Add, Sub, and overflow checking operations, write a simulation program for 1-bit ALU in 80x86 assembly language. In Phase1, include the following three functionalities in the 1-bit ALU:

AND, OR, and Add

Subtraction and overflow checking functionalities will be included in Phase2.

As explained in the class, the simulation granularity is the following 4 sub-components:

AND gate, OR gate, 1-bit full adder, and 4x1 multiplexor

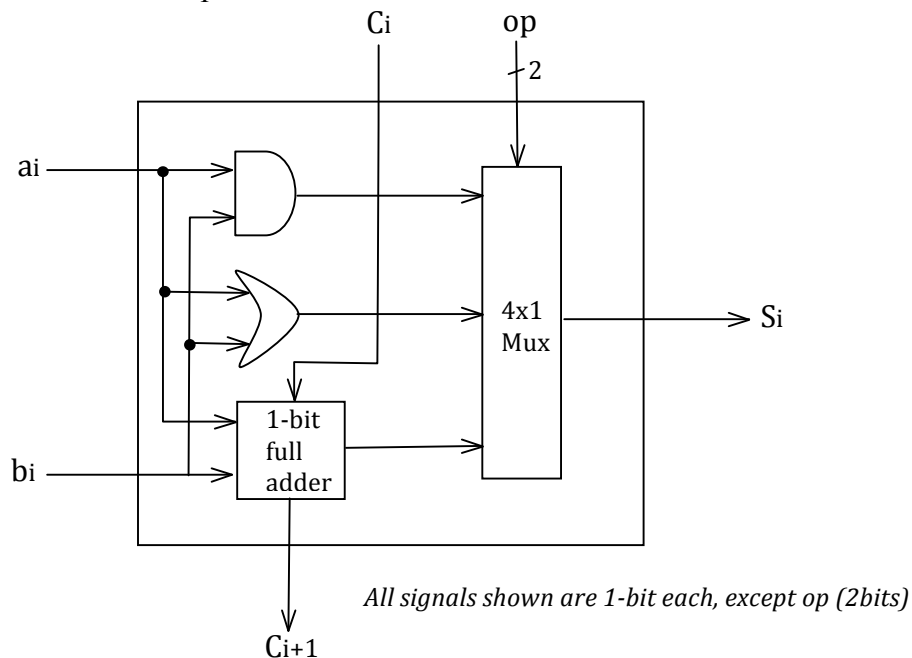
Your 1-bit ALU simulator should have the above four sub-components as procedures (with parameters). You should also define a procedure for the 1-bit ALU (with parameters) and the main program (driver) calls it with passing argument values.

The 1-bit ALU is controlled by op signal, i.e.,

op (2bits): 00 – AND operation

01 – OR operation

10 – Add operation

**Suggested steps:**

Step1. Define procedures for AND gate, OR gate, 1-bit-full adder, and 4x1 Mux;

Test each sub-component for the correctness of the logic, before implementing Step2.

Step2. Define a procedure for the 1-bit ALU module, which calls the sub-components.

Step3. Write the main driver code, which prompts and accesses input values; calls the 1-bit ALU procedure by passing input values to parameters; displays input/output values in an appropriate format.

**Submission:**

Include good documentations in the code (global doc. and each procedure head doc.) and

- submit hardcopies of the source code and run time output.
- Also send your source code by Email to [jpark@csufresno.edu](mailto:jpark@csufresno.edu)

Test run data is shown in the next page.

Test run data (input values) – please use these values for the output submission:

ai bi ci op

0 0 0 00 --- your output msg box should include these 4 input values and outputs (Si, Ci+1)

0 1 1 00

1 0 0 00

1 1 1 00

-----

0 0 1 01

0 1 0 01

1 0 1 01

1 1 0 01

-----

0 0 0 10

0 0 1 10

0 1 0 10

0 1 1 10

1 0 0 10

1 0 1 10

1 1 0 10

1 1 1 10